

1 GEOMETRIC MEAN DISTANCE $D_m = \sqrt[n]{\prod_{i=1}^n D_{ij}}$; n - conductors in one bundle; m - conductors remaining;


GEOMETRIC MEAN RADIUS $D_s = \sqrt{\prod_{i=1}^n \prod_{j=1}^m D_{ij}}$; note D_{kk} where $k = 1, 2, \dots, n$ has skin effect

RADIUS WITH SKIN EFFECT $r' = r e^{(-k_s \frac{r}{\pi})}$; k_s - $\frac{1}{4}\pi$ skin effect correction; r - actual radius


GEOMETRIC MEAN RADIUS FOR CAPACITANCE $D_{eq} = D_s$ without the skin effect i.e remove $[e^{-k_s \frac{r}{\pi}}]$

$$L' = \frac{M_0}{2\pi} \ln \left[\frac{D_m}{D_s} \right] \left(\frac{1}{l/m} \right); \quad C' = \frac{2\pi \epsilon_0}{\ln \left[\frac{D_m}{D_{eq}} \right]} \left(\frac{1}{l/m} \right); \quad R' = k_s \rho \frac{l}{A} \left[\frac{1}{l/m} \right]; \quad A = \pi r^2$$

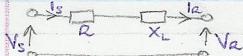3 SHORT LINES: $l < 50$; $R = R' l$; $X_L = \omega L' l$; $A = 1 \angle 0$; $B = R + jX_L$



MEDIUM LINES: $50 < l < 200$

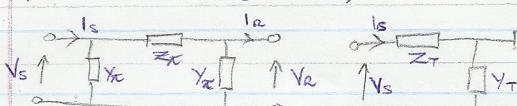

$$Z_\pi = (R' + j\omega L')l; \quad Y_\pi = (C' + j\omega C')l$$

$$Z_T = (R'_T + j\omega L'_T)l; \quad Y_T = (C'_T + j\omega C'_T)l$$


use $C'_T = 0$ infinite resistance w.r.t. ground

$$A = 1 + Z_\pi Y_\pi; \quad B = Z_\pi$$

$$\text{LONG LINES: } l > 200 \quad \gamma = \sqrt{(R' + j\omega L')(C' + j\omega C')}; \quad Z_0 = \sqrt{\frac{(R' + j\omega L')}{(C' + j\omega C')}}.$$

$$Z_\pi = Z_0 \sinh(\gamma l); \quad Y_\pi = \frac{\cos(\gamma l) - 1}{Z_0}; \quad Y_T = \frac{\sinh(\gamma l)}{Z_0}; \quad Z_T = \frac{\cosh(\gamma l) - 1}{Y_T}$$
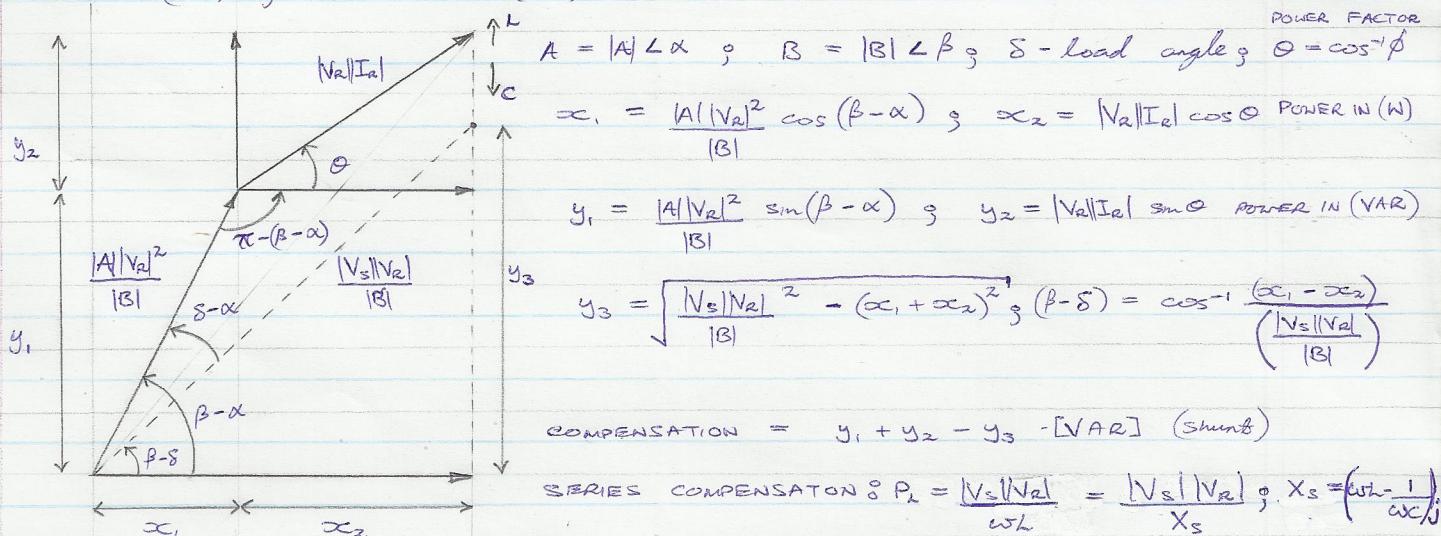
$$A = \cosh(\gamma l); \quad B = Z_0 \sinh(\gamma l)$$




5 FAULT LEVEL = $\frac{\text{MVA}_{\text{base}}}{\text{total impedance [upstream]}} [\text{MVA}]$; FAULT CURRENT = $\frac{\text{MVA}_{\text{fault level}}}{\sqrt{3} V_{\text{base}} (\text{@ fault point})} [\text{A}]$

RATED CURRENT = $\frac{\text{rated MVA of transformer}}{\sqrt{3} V_{\text{at the bus}}} [\text{A}]$; CURRENT MULTIPLIER = $\frac{I_{\text{rated}}}{I_{\text{pickup}}}$

I_{pickup} is the current @ which the IDMT responds; $t = \frac{0.14}{I_{\text{pickup}}^{0.02} - 1} \times \text{time multiplier}$

$$I_{\text{pu}} = \frac{I_{\text{fault}}}{I_{\text{rated}}}$$

①

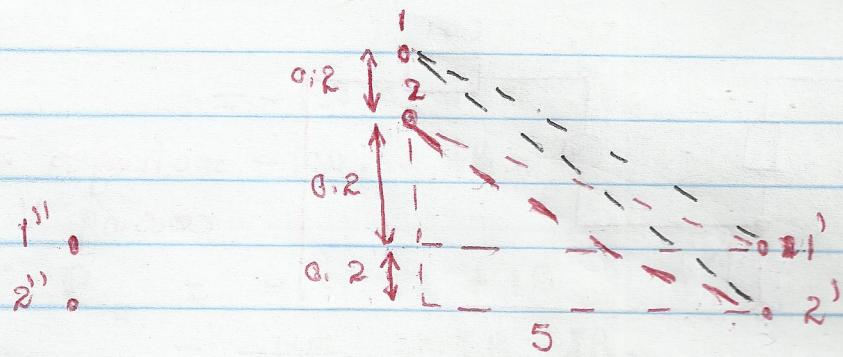

$$D_{11}^{(1)} = 5.02 = D_{22}^{(1)}$$

$$D_{12}^{(1)} = 5.04 \quad D_{21}^{(1)} = 5.004$$

$$G.M.D = \sqrt[2x4]{(5.02 \times 5.02 \times 5.004 \times 5.04)^2}$$

$$= \underline{5.021 \text{ m}}$$

$$D_{11}^{(2)} = 10, \quad D_{22}^{(2)} = 10$$

$$D_{12}^{(2)} = D_{21}^{(2)} = 10.002$$

$$G.M.D = \sqrt[8]{5.02 \times 5.02 \times 5.04 \times 5.004 \times 10 \times 10 \times 10.002 \times 10.002}$$

$$= 7.086 \text{ m.}$$


PTP 2012

(2)

↓ 200 mm

↑

1.

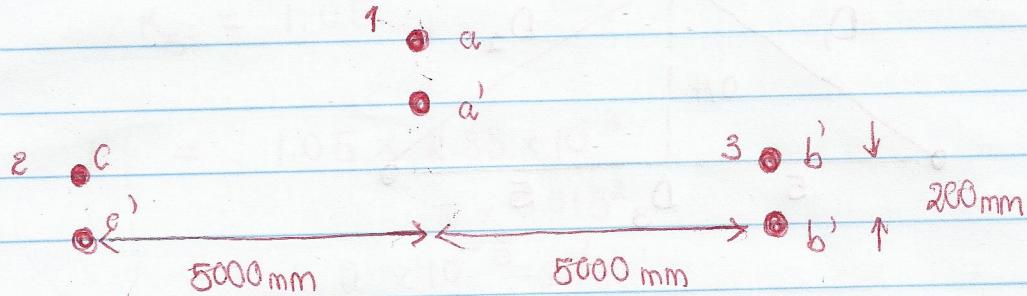

$$\text{radius} = 15 \text{ mm}$$

$$G.M.R = \sqrt[2]{aa \times aa' \times a'a \times a'a'} \quad \text{or} \quad \sqrt[2]{aa \times aa'}$$

$$aa' = a'a' = r(-K_s \mu_r/4)$$

$$m = \sqrt{\frac{2\pi(50) \times 4\pi \times 10^{-7}}{2.83 \times 10^{-8}}} = 118.11 \quad \mu_r = 1$$

$$mr = 118.11 \times 0.015 = 1.772$$

$$K_s = 0.975$$


$$aa = a'a' = 0.015 \text{ e}^{-0.975/4} \\ = 0.0118 \text{ m}$$

$$aa' = a'a = 0.2 \text{ m}$$

$$G.M.R = \sqrt[4]{0.0118^2 \times 0.2^2} \\ = 0.0486 \text{ m}$$

Assuming distance btwn subconductors is << distance btwn conductors (phase)

$$G.M.D = \sqrt[3]{D_1 D_2 D_3}$$

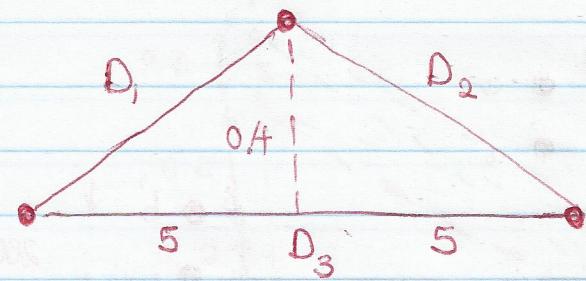

$$D_1 = 5.016 \text{ m} = D_2 \quad D_3 = 10 \text{ m.}$$

$$G.M.D = \sqrt[3]{5.016^2 \times 10} = 7.08 \text{ m.}$$

$$\begin{aligned} L' &= 2 \times 10^{-7} \ln \left(\frac{7.086}{0.0486} \right) \\ &= 9.96 \times 10^{-7} \text{ H/m.} \end{aligned}$$

$$C' = \frac{2\pi\epsilon_0}{\ln \left(\frac{7.086}{D_{eq,lc}} \right)}$$

$$D_{eq,lc} : aa = a'a' = 0.015 \text{ } \cancel{m} \quad (\text{no skin effect})$$

$$= 0.017 \text{ m.}$$

~~$$D_{eq,lc} = \sqrt[4]{0.017^2 \times 0.2^2}$$~~

$$= 0.0484 \text{ m.}$$

~~$$D_{eq,lc} = \sqrt[4]{0.015^2 \times 0.2^2}$$~~

~~$$D_{eq,lc} = 0.048 \text{ m.}$$~~

$$\therefore C' = 1.115 \times 10^{-11} \text{ F/m.}$$

~~$$C' = 20.1 \times 10^{-12} \text{ F/m.}$$~~

$$= 11.4 \text{ pF/m}$$

~~$$C' = 20.1 \text{ pF/m.}$$~~

$$R' = K_s \frac{\rho}{A}$$

~~$$C' = 11.4 \text{ PF}$$~~

(4)

$$K_s = 1.05$$

$$R' = \frac{1.05 \times 2.88 \times 10^{-8}}{\pi \times 0.015^2} \\ = 4.2 \times 10^{-5} \Omega/m$$

b) $L' = 2 \times 10^{-7} \ln\left(\frac{D_m}{D_{eq}}\right)$

For conductor bundles D_{eq} increase D_{eq} values \Rightarrow in turn L'


c) For a symmetrically spaced 3 ϕ conductor geometry.

2 An overhead line has a higher $\frac{X}{R}$ ratio than similarly rated cable because there is flux cancellation in rated cables becoz their spacing is small compared to overhead cables where there is significant flux cancellation due to a larger separation distance between phase conductors.

$$L = 2 \times 10^{-7} \ln\left(\frac{D_m}{D_{eq}}\right) \quad \text{--- (1)}$$

From (1), $D_m \gg D_{eq} \Rightarrow L$ is high. $\Rightarrow X$ is high as well, compared to rated cables in $\Rightarrow D_m/D_{eq}$ is very small.

b)

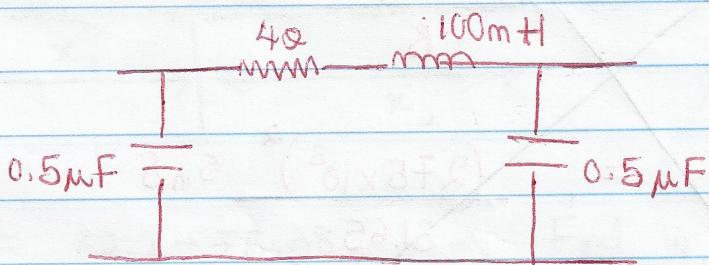

(5)

$$V = 200 \text{ kV} \quad 275 \text{ kV}, \quad P_R = 300 \text{ MW}, \quad \text{pf} = 0.94 \text{ lagging}$$

$$A = 1 + Z_{\pi} Y_{\pi}$$

$$B = Z_{\pi}$$

$$\begin{aligned} Z_{\pi} &= (R' + j\omega L') l = R'l + j\omega L' \\ &= 4\omega + j 100 \text{ mH} \times 2\pi f \\ &= 4\omega + j 10\pi \\ &= 4\omega + j 31.4\omega \end{aligned}$$

$$\begin{aligned} Y_{\pi} &= \frac{(G' + j\omega C')l}{2} = \frac{G'l + j\omega C'l}{2} \quad (G=0) \\ &= \frac{j 2\pi (50) \times 0.5 \times 10^{-6}}{2} \\ &= j 78.54 \times 10^{-6} \text{ S} \end{aligned}$$

$$B = 4 + j 31.4 = 31.65 \angle 82.7^\circ$$

$$\begin{aligned} A &= 1 + (31.65 \angle 82.7^\circ)(78.54 \times 10^{-6} \angle 90) \\ &= 1 + 2.49 \times 10^{-3} \angle 172.7 \\ &= 0.9975 + j 816 \times 10^{-6} \\ &= 0.9975 \angle 0.018 \end{aligned}$$

$$V_S = A V_R + B I_R$$


NB

$$\text{Load Real Power} = \frac{|V_S| |V_R| \sin \delta}{B}$$

$$\left(\frac{300}{3} \right) = \frac{(275 \times 10^3)^2}{31.65} \sin \delta$$

$$\sin \delta = 41.9 \times 10^{-9}$$

(6)

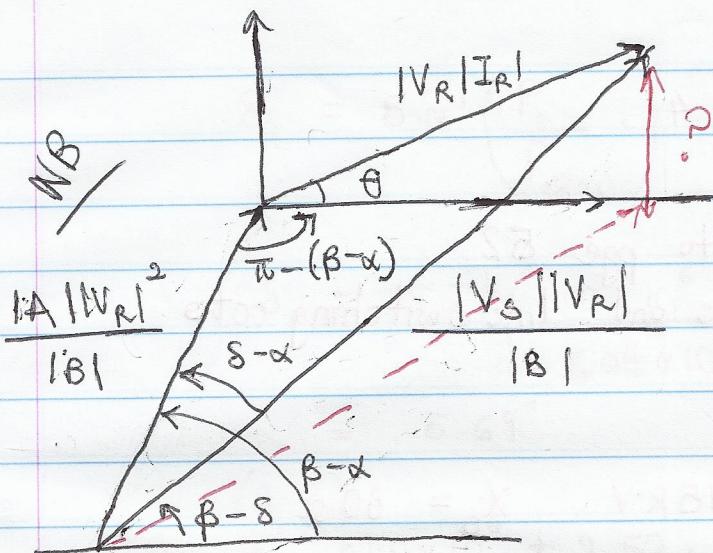

$$\theta = 19.95^\circ = \cos^{-1}(0.94)$$


$$\frac{|A| |V_R|}{|B|}^2 = \frac{0.9975 \times (275 \times 10^3)}{31.65}$$

$$= 2.38 \text{ MVA}$$

$$= 2.38 \text{ GVA}$$

$$\frac{|V_s| |V_R|}{|B|} = \frac{(275 \times 10^3)^2}{31.65} = 2.39 \times 10^9 \text{ VA}$$
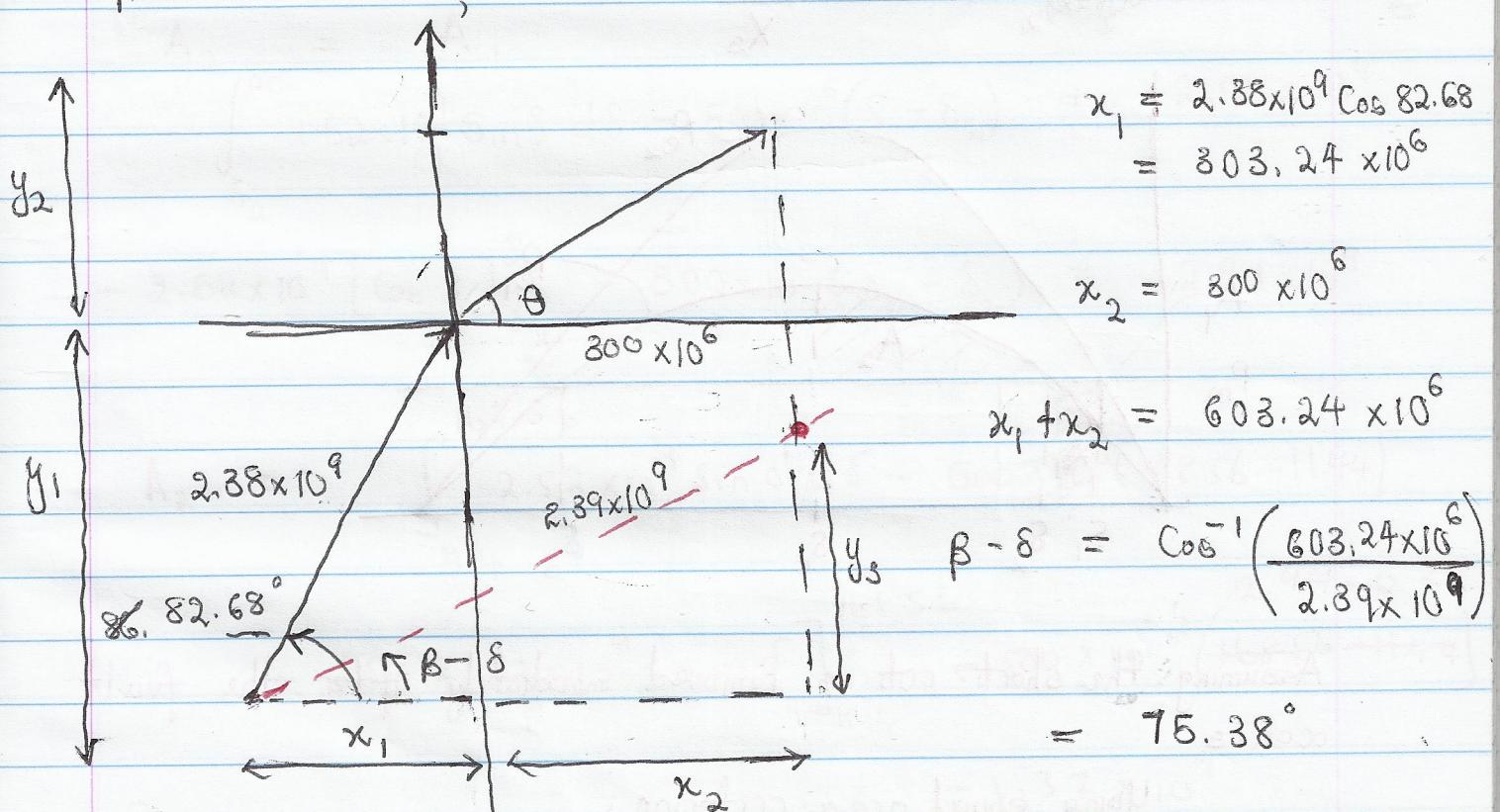
$$\beta = 82.7^\circ, \alpha = 0.018^\circ$$



$$\therefore \delta = 82.7 - 75.38 \Rightarrow \text{Find } y_1, y_2 \text{ and } y_3 \text{ by resolving into the vertical.}$$

$$= 7.32^\circ$$

Continued on page 11

(11)

$$\begin{aligned}y_1 &= 2.38 \times 10^9 \sin 82.68 = 2.36 \times 10^9 \text{ VAR} \\y_2 &= 300 \times 10^6 \tan 19.95 = 108.89 \times 10^6 \text{ VAR} \\y_3 &= 2.39 \times 10^9 \sin 75.38 = 2.31 \times 10^9 \text{ VAR}\end{aligned}$$

$$\text{Required VAR} = y_1 + y_2 - y_3$$

$$= 158.89 \text{ MVAR}$$

$$P = \frac{V_r^2}{X_c} = \frac{V_r^2}{2\pi f C}$$

$$\begin{aligned}C &= \left(\frac{V^2}{2\pi f P} \right) \\&= \frac{(275 \times 10^8)^2}{(2\pi \times 50 \times 158.89 \times 10^6)} \\&= 1.515 \text{ F} \quad (\text{check})\end{aligned}$$

SIL Defn: Refer to the book, pg 4

$$\text{if } P_L > \text{SIL} \rightarrow V_R < V_s$$

$$\text{if } P_L < \text{SIL} \rightarrow V_R > V_s$$

2010

$$P_L = \frac{V^2}{X_s}$$

$$\text{where } X_s = \cancel{\omega L} \quad \left| j(\omega L - \frac{1}{\omega C}) \right| = \omega L - \frac{1}{\omega C}$$

$$P = 600 \text{ MW}$$

$$P_{\text{New}} = P + 0.2P = 1.2P = 720 \text{ MW}$$

NB

$$X_s = \frac{V^2}{P}$$

$$= \frac{(400 \times 10^3)^2}{\frac{1}{3} (720 \times 10^6)}$$

$$= \frac{222.222}{wC}$$

$$2\pi \times 80 \times 475 \times 10^{-3} - \frac{1}{wC} = 222.222$$


??

Stability

3a. Transient stability refers to the ability of a power system to regain equilibrium after a significant disturbance occurs in the power system.

bi Series Compensation }
Shunt Compensation } last adv and disadv

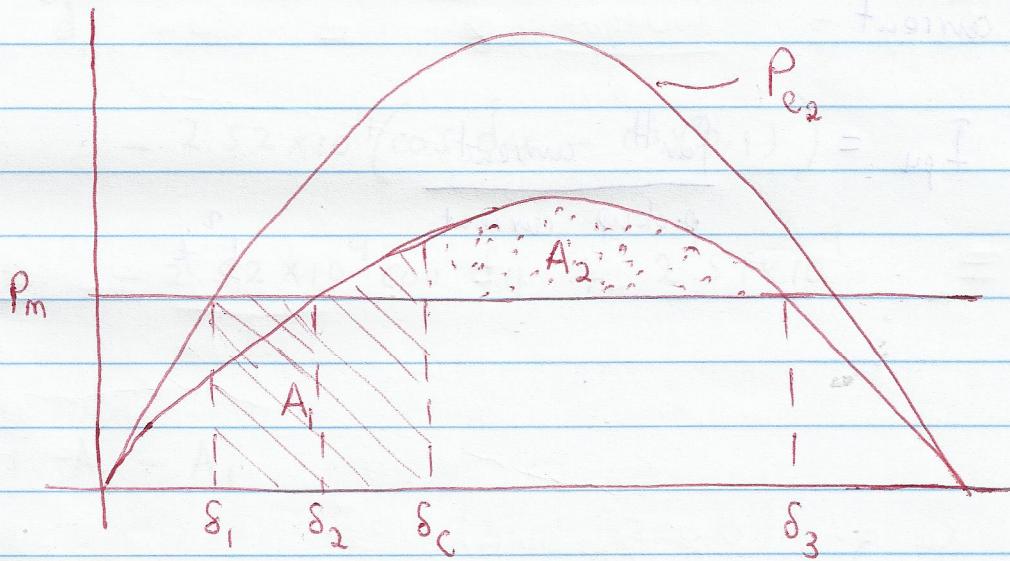c) $P_m = 500 \text{ MW}$, $V_b = V_R = 275 \text{ kV}$, $X_s = 80 \Omega$




$$A_2 = 3.57 \times 10^9$$

$$A_1 = \int_{d_1}^{d_2} (P_s - P_{\text{exmax}} \sin \delta) d\delta$$

$$= \int_{0.1}^{0.2} (500 \times 10^6 - 2.52 \times 10^9 \sin \delta) d\delta$$

$$= 500 \times 10^6 (0.2 - 0.1) + 2.52 \times 10^9 (\cos 0.2 - \cos 0.1)$$

$$= 12.6 \times 10^6$$

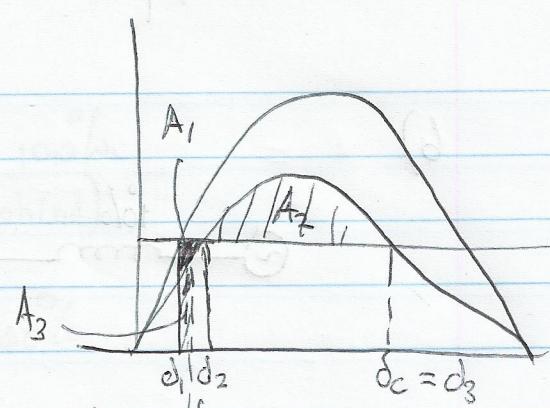

$$A_3 = \int_{d_1}^{d_4} P_{\text{exmax}} \sin \delta d\delta$$

$$= \int_{d_1}^{d_4} 2.52 \times 10^9 \sin \delta d\delta$$

$$= -2.52 \times 10^9 (\cos \delta_4 - \cos(0.1))$$

$$\approx -2.52 \times 10^9 \cos \delta_4 + 2.51 \times 10^9$$

$$A_3 = A_2 - A_1$$


$$-2.52 \times 10^9 \cos \delta_4 = 3.57 \times 10^9 - 12.6 \times 10^6 - 2.5 \times 10^9$$

$$\cos \delta_4 = -\frac{1.047 \times 10^9}{2.52 \times 10^9}$$

$$\delta_4 = 1.14 \text{ rad}$$

14

6) Question 6 (2012)

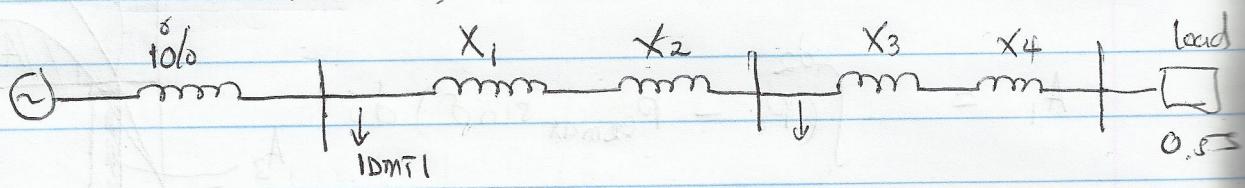

$$X_{1pu} = \frac{100 \text{ MVA}}{20 \text{ MVA}} \times 10\% = 50\%$$

$$Z_{base} = \frac{(V_{base})^2}{MVA_{base}} = \frac{(6.6 \times 10^3)^2}{100 \text{ MVA}} = 0.4356$$

$$X_{2pu} = 1/0.4356$$

$$= 229.5\%$$

$$X_{3pu} = \frac{100 \text{ MVA}}{5 \text{ MVA}} \times 10\% = 160\%$$

$$Z_{base} \text{ at bus 2} = \frac{(V_{base})^2}{MVA} = \frac{(400)^2}{100 \text{ MVA}} = 0.0016$$

$$X_{4pu} = (0.005/0.0016) \times 100\%$$

$$= 312.5\%$$

14

61

15

IDMT 1

$$\text{Fault level (MVA)} = \frac{\text{MVA}_{\text{base}} \times 100\%}{\text{Total impedance (behind)}}$$

$$= \frac{100 \text{ MVA} \times 100\%}{10\%}$$

$$= 1 \times 10^9 \text{ V} = 1000 \text{ MVA}$$

$$\text{Fault current} = \frac{\text{Fault level (MVA)}}{\sqrt{3} V_{\text{bus}} \text{ (connected to the fault point)}}$$

$$= \frac{1000 \text{ MVA}}{\sqrt{3} (132 \text{ kV})}$$

$$A_{24} = 4.37 \text{ kA}$$

$$\text{Rated current} = \frac{\text{rated MVA of transformer}}{\sqrt{3} V_{\text{at the bus}}}$$

$$= \frac{20 \text{ MVA}}{\sqrt{3} (132 \text{ kV})}$$

$$= 87.5 \text{ A}$$

Current transformer ratio becomes 100:1 / 100:5

If primary current = 87.5 A, secondary current = 0.875 A

$$\text{Current multiplier} = \frac{\text{rated current}}{1.25 (\text{rated current})}$$

$$\text{current multiplier} = \frac{0.875 \text{ A}}{1.25 \times 0.875} = 0.8$$

$$t = \frac{0.14}{I_{pu} - 1} \times \text{time multiplier}$$

$$t = 0.5 + 0.5 + 0.5 =$$

$$= 1.5 \text{ s}$$

$$\text{time multiplier} = \frac{t (I_{pu} - 1)^{0.02}}{0.14}$$

$$= \frac{1.5 (49.94 - 1)^{0.02}}{0.14}$$

$$= 0.872$$

$$I_{pu} = \frac{\text{Fault current}}{\text{rated current}} = \frac{4.37 \text{ kA}}{875 \text{ A}}$$

$$\text{transformer to AVM} = 49.94$$

When there is no fuse

$$I^2 t = \text{KA}_{\text{eff}}$$



fault current

A7F8.0 = transformer primary, A7.F8 = primary winding fault

A7F8.0 = transformer primary, A7.F8 = primary winding fault


$$8.0 = \frac{1}{A7F8.0}$$

$$8.0 = \frac{1}{A7F8.0 \times 25.1}$$

= 25.1 hours

(7)

2010

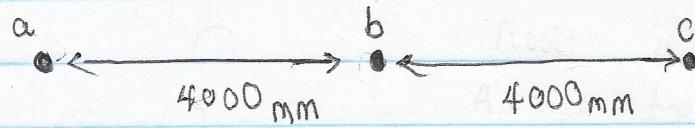

$$\begin{aligned} \text{G.M.D} &= \sqrt{ab \times ac} \\ &= \sqrt{4 \times 8} \\ &= 5.66 \text{ m.} \end{aligned}$$

For Inductance: $-k_0 \mu_r / 4$

$$\text{G.M.R} = r_e$$

$$m = \sqrt{\frac{2\pi \times 50 \times 4\pi \times 10^{-7}}{2.83 \times 10^{-8}}}$$

$$m = 0.118.11$$

$$\mu_r = 118.11 \times 0.015 = 1.772$$

$$K_0 = 0.975$$

$$\begin{aligned} \text{G.M.R} &= 0.015 \text{ m} \\ &\quad -0.975 \times 1/4 \\ &= 0.0118 \text{ m.} \end{aligned}$$

$$\begin{aligned} L' &= 2 \times 10^{-7} \ln \left(\frac{5.66}{0.0118} \right) \\ &= 1.23 \mu\text{H/m.} \end{aligned}$$

For Capacitance:


$$\text{G.M.R} = 0.015 \text{ m}$$

(8)

$$C' = \frac{2\pi \times 8.85 \times 10^{-12}}{\ln \left(\frac{5.66}{0.015} \right)} \\ = 9.37 \mu F/m.$$

$$R' = K_s \frac{P}{A}$$
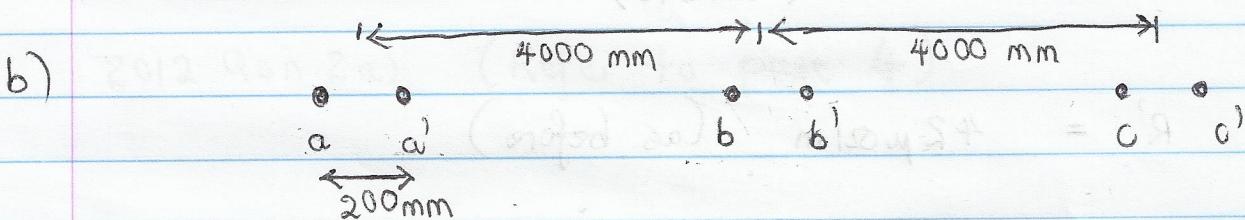
$$= \frac{1.05 \times 2.83 \times 10^{-8}}{\pi \times 0.015^2} = 42 \mu \Omega / m.$$



$$ab = 4 \text{ m}, ab' = 4.200 \text{ m}, ac = 8 \text{ m}, ac' = 8.200 \text{ m} \\ a'b = 3.8 \text{ m}, a'b' = 4 \text{ m}, a'c = 7.8 \text{ m}, a'c' = 8 \text{ m}.$$

$$G.M.D = \sqrt[8]{ab \times ab' \times ac \times ac' \times a'b \times a'b' \times a'c \times a'c'} \\ = 4.86 \text{ m.}$$

Inchustance :

$$m = \sqrt{\dots} = 118.11$$

$$mr = 1772, K_s = 0.975 \\ r' = 0.015 \text{ m} = 0.0118 \text{ m.}$$

$$G.M.R = \sqrt[4]{0.0118^2 \times 0.2^2} = 0.0486 \text{ m.}$$

(9)

$$L' = 2 \times 10^{-7} \ln \left(\frac{4.86}{0.0486} \right) = 899.82 \text{ nH/m}$$

Capacitance :

$$Q.M.R = \frac{4\pi \times 0.015^2 \times 0.2^2}{0.0548} = 0.0548 \text{ m.}$$

$$C' = \frac{2\pi \times 8.85 \times 10^{-12}}{\ln \left(\frac{4.86}{0.0548} \right)} = 12.7 \text{ nF/m.}$$

$$R' = 42 \mu\Omega/\text{m} \text{ (as before)}$$

Power limit, $P_{\text{lim}} = \frac{V_s V_R}{\omega L} = \frac{182000^2}{\omega L' l}$

(i) $L' = 1.23 \mu$ $P_{\text{lim}} = \frac{182000^2}{2\pi \times 50 \times 1.23 \times 10^{-6} \times 200 \times 10^3} = 225.5 \text{ MW}$

NB
(ii) $L' = 899.82 \text{ nH}$ $P_{\text{lim}} = \frac{182000^2}{2\pi \times 50 \times 1.23 \times 10^{-6} \times 899.82 \times 10^{-9} \times 200 \times 10^3} = 308.4 \text{ MW}$

(11)

(10)

$$L = \frac{\mu_0}{2\pi} \ln \left(\frac{D_m}{D_s} \right)$$

No ~~def~~ linear relationship.

Advantages

- Increasing power limit
- More real power compared to reactive
- Increase loadability of the line
- Check scanned paper (tuts)

2012 Qsn 2a) (Refer to page 4)

$$R_1 = \frac{1.15 \times 1.77 \times 10^{-8}}{\pi \times (20 \times 10^{-3})^2}$$

$$= 5.09 \times 10^{-5} \Omega/m.$$

$$R = R_1 + R_2 + R_3$$

$$= 1.58 \times 10^{-4} \Omega/m.$$

Question 2: Advantages of Bundles.

- Bundled conductors are primarily employed to reduce the corona loss and radio interference.
- 1. Bundled conductors / phase reduces the voltage gradient in the vicinity of the line. Thus reduces the possibility of the corona.
- 2. Improvement in the transmission efficiency as loss due to corona effect is ~~is~~ countered.
- 3. Bundled conductor lines will have higher capacitance to neutral in comparison w single lines. Thus they will have higher charging currents which helps in improving the power factor.
- 4. Bundled conductor lines have higher C and lower L than ordinary lines. They will have a higher S/L [Z = (L/C)^{1/2}]. Higher S/L will have higher maximum power transfer ability.
- 5. With increase in self GMD or GMR inductance / phase will be reduced compared to single conductor line. This results in lesser reactance / phase compared to the ordinary single line. Hence lesser loss due to reactance drop.

3. $I \rightarrow J \rightarrow E \rightarrow V$

$$J = \frac{I}{A} = \frac{I}{2\pi r \delta}$$

$$E = \frac{J}{\delta} = \frac{I}{2\pi r \delta}$$