

Question 1

AMC1021S static characteristics:

Operating temperature	-55°C to 150°C
Input Range	-6 gauss to 6 gauss
Linearity	$\pm 1.6\%$ FS
Hysteresis	$\pm 0.08\%$ FS
Bridge Offset	11.25 mV
Sensitivity	1.25 mV/V/gauss
Noise Density	48 nV/ $\sqrt{\text{Hz}}$
Resolution	85 μgauss
Sensitivity Temperature Coefficient	-0.32%/°C
Bridge Offset Temperature Coefficient	$\pm 0.05\%$ /°C
Bridge Ohmic Temperature Coefficient	0.25 %/°C \leftarrow no effect
Cross-Axis effect	0.3 % FS

LMV324N static characteristics

Offset Voltage (input)	9 mV
Bias Current	500 nA
Offset current (input)	150 nA
CMRR	65 dB
PSRR	60 dB
Output Swing	400 mV

* There is a fundamental error with the circuit shown in Figure 6 in that it can only have an input range of ± 2.5 gauss. There are two ways I could address this problem:

- 1) Limit the system specifications to ± 2.5 gauss.
- 2) Change resistors $R5$ and $R6$ to reduce the gain to allow for ± 5 gauss.

I'll go with option 2 $\therefore R5 - R6 = 10k52 \pm 0.5\%$
 $\therefore \text{Gain} = 100$

System Input Range ± 5 gauss
 System Operating Temperature 15°C to 25°C

Error Due to HMC1021 S:

$$\text{Resolution} = 85 \mu\text{V/gauss} \Rightarrow \frac{85 \mu\text{V}}{5} \times 100\% = 0.0017\% \text{ FS}$$

$$\text{Bridge Offset} = 11.25 \text{ mV} \Rightarrow \frac{11.25 \text{ mV} \times 100^{\text{gain}}}{5 \text{ V}} = 22.5\% \text{ FS}$$

$$\text{Sensitivity error} = \frac{1.25 - 1}{1} \times 100\% = 25\% \text{ FS}$$

Calibration table shows 1 mV/V/gauss

$$\text{Noise density} = 48 \times 10^{-9} \text{ V} \times \sqrt{10000} = 4.8 \times 10^{-6} \text{ V} \Rightarrow 0.0096\% \text{ FS}$$

$$\text{Linearity} = 1.6\% \text{ FS}$$

$$\text{Hysteresis} = 0.08\% \text{ FS}$$

(3)

Sensitivity Temperature coefficient: $\Delta T = 25^\circ\text{C} - 15^\circ\text{C}$
 $= 10^\circ\text{C}$

$$\hookrightarrow = -0.32\% (10) \\ = -3.2\%$$

Bridge offset temperature coefficient: $0.05\% (10)$
 $= 0.5\%$

Cross-Axis effect = $0.3\% \text{ FS}$

$$V_o = 1 + \overset{\text{bridge offset}}{0.225} \overset{\text{temperature drift}}{(1.005)} + \overset{\text{resolution}}{0.000017} + \overset{\text{noise}}{0.000016} + \overset{\text{linearity}}{0.016} + \overset{\text{hysteresis}}{0.0008}$$

Ideal straight line:

$$V_o = 5V \times 1 \text{ mV/V/gauss} (\gamma)$$

Introducing error

$$V_o(\gamma) = \left[\left(5V \times 1 \frac{\text{mV}}{\text{V/gauss}} \overset{\text{temperature drift}}{(1-0.032)} \right) \left(\gamma \overset{\text{resolution}}{\left(1 + \frac{0.000017}{2} \right)} \right) + \overset{\text{bridge offset}}{11.25 \text{ mV}} + \overset{\text{noise}}{4.8 \times 10^{-6} \text{ V}} \right] \times \left\{ \overset{\text{linearity}}{(1 + 0.016)} + \overset{\text{hysteresis}}{0.0008} + \overset{\text{cross-axis}}{0.003} \right\}$$

FS @ $\gamma = 5 \text{ gauss}$


ideally $V_o = 25 \text{ mV}$

Actually:

$$V_o(5 \text{ mm}) = 36.16 \text{ mV}$$

$$\text{error} = 44.63\%$$

Error due to Amp:

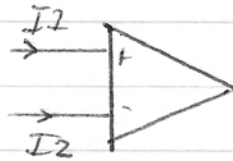

$$I_{Bias} = \frac{I_1 + I_2}{2}$$


$$I_{offset} = I_1 - I_2$$

$$\therefore I_1 = I_{Bias} + I_{offset}/2$$

$$I_2 = I_{Bias} - I_{offset}/2$$

$I_1 = 575 \text{ nA}$
 $I_2 = 425 \text{ nA}$

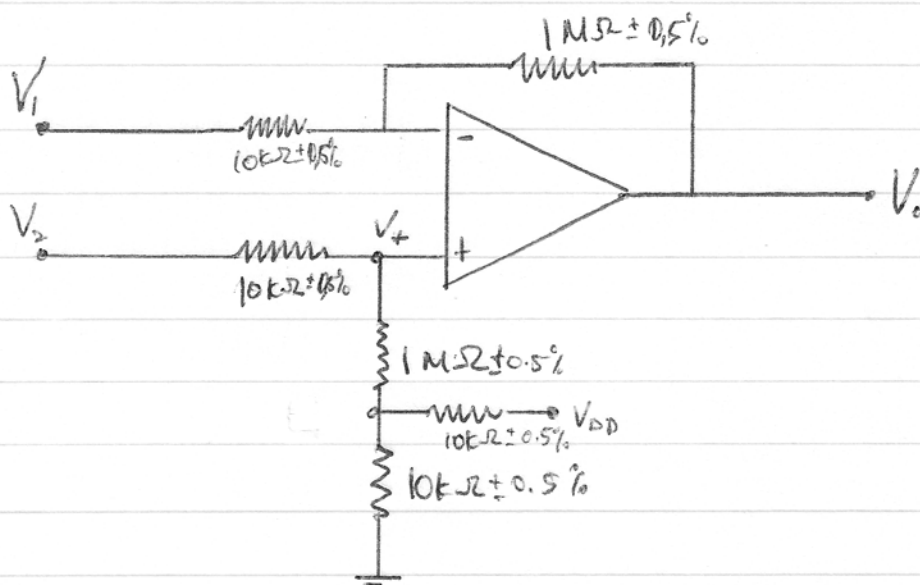} considering we're working with mV these may be significant.



(5)


Super position

① Short V_{DD} :

$$V_+ = V_2 \left(\frac{1M\Omega + \frac{10k\Omega \cdot 10k\Omega}{10k\Omega + 10k\Omega}}{1M\Omega + \frac{10k\Omega \cdot 10k\Omega}{10k\Omega + 10k\Omega} + 10k\Omega} \right)$$

$$= 0.990147 \dots V_2$$

$$= 0.99 V_2$$

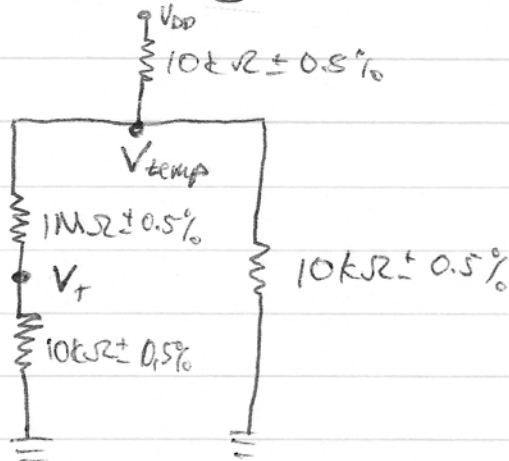② Short V_2 :

$$R_{||} = 9902 \Omega$$

$$\therefore V_{temp} = V_{DD} \left(\frac{9.902 k\Omega}{10k\Omega + 9.902 k\Omega} \right)$$

$$V_+ = \frac{1M\Omega}{1M\Omega + 10k\Omega} V_{DD} \left(\frac{9.902 k\Omega}{10k\Omega + 9.902 k\Omega} \right)$$

$$= 0.493 V_{DD}$$

$$\therefore V_+ = 0.99 V_2 + 0.493 V_{DD}$$

this is using ideal resistors...

(6)

So the output would be:

$$\frac{V_i - V_+}{10k\Omega} = \frac{V_+ - V_o}{1M\Omega}$$

$$100(V_i - V_+) - V_+ = -V_o$$


$$\therefore V_o = 100(V_+ - V_i) + V_+$$

$$= 101V_+ - 100V_i,$$

$$= 99.99V_2 + 45.743V_{DD} - 100V_i \quad (\text{Ideally})$$

So at full scale we have $V_i = 5mV$ and $V_2 = 0mV$

$$\therefore V_o =$$

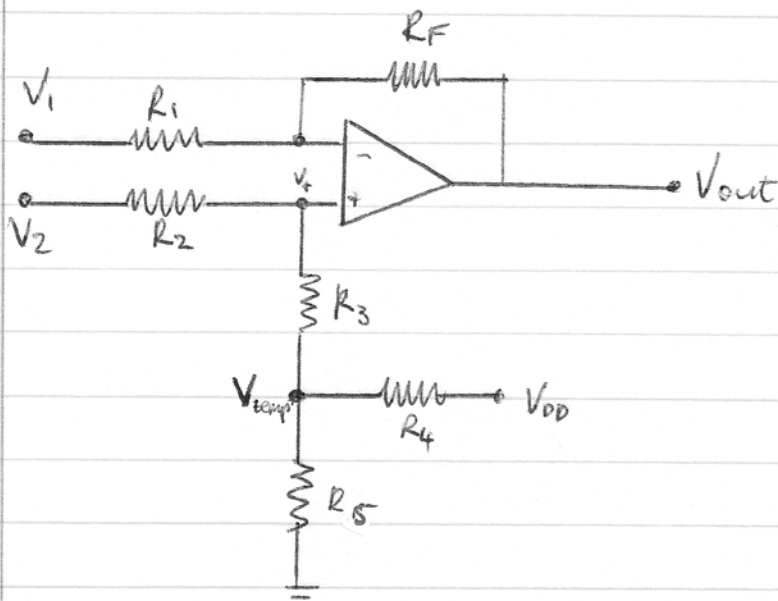

If $R_4 = R_5 \ll R_3$ assume $V_{temp} = V_{DD}/2$

~~Superposition for V_+ :~~

$$\begin{aligned} \text{Now } V_+ &= (V_2 - V_{temp}) \left(\frac{R_3}{R_2 + R_3} \right) \\ &= (V_2 - V_{DD}/2) \left(\frac{R_3}{R_2 + R_3} \right) \end{aligned}$$

$$V_{out1} = \left(1 + \frac{R_F}{R_1} \right) (V_2 - V_{DD}/2) \left(\frac{R_3}{R_2 + R_3} \right)$$

$$V_{out2} = - \frac{R_F}{R_1} V_1$$

$$\begin{aligned} V_{out} &= (V_2 - V_{DD}/2) \left(1 + \frac{R_F}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} \right) - \frac{R_F}{R_1} V_1 \\ &= 100 (V_2 - V_{DD}/2) - 100 V_1 \end{aligned}$$

(8)

From A.3.10 TI Op amps for Everyone

$$V_o = V_2 \left(\frac{R_F + R_1}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} \right) + V_{temp} \left(\frac{R_F + R_1}{R_1} \right) \left(\frac{R_2}{R_2 + R_3} \right) - V_1 \frac{R_F}{R_2}$$

$$= 100V_2 + V_{temp} - 100V_1$$

$$= 100(V_2 - V_1) + V_{temp}$$

$$= 100(V_2 - V_1) + V_{DD}/2$$

I know max difference is 25mV

$$\therefore V_2 - V_1 = 25\text{mV} \quad (\text{ideally})$$

$$V_{DD} = 5\text{V} \quad \text{ideally}$$

$$\therefore V_o = 100(25\text{mV}) + 2.5\text{V} = 5\text{V} \quad \text{ideal!}$$

Introducing errors

Make R_F big

R_1 small

R_2 small

R_3 big

(9)

Assuming we're at 15°C and resistors have zero temp drift @ 25°C

~~$$R_F = 1\text{M}\Omega (1.005) (1 \pm 25 \times 10^{-6})$$~~

$$R_F = 1\text{M}\Omega \left(1 + \overset{\text{tolerance}}{0.005} - \overset{\text{temp drift}}{25 \times 10^{-6} \times 10} \right)$$

$$= 1.00475\text{M}\Omega$$

$$R_1 = 10\text{k}\Omega \left(1 - 0.005 - 25 \times 10^{-6} \times 10 \right)$$

$$= 9.9475\text{k}\Omega$$

$$R_2 = 9.9475\text{k}\Omega$$

$$R_3 = 1.00475\text{M}\Omega$$

Now

$$V_o = 101.005 V_2 + V_{\text{temp}} - 101.005 V_1$$

$$= 101.005 (V_2 - V_1) + V_{\text{temp}}$$

Introduce amp errors

$$V_o = 101.005 (V_2 - V_1) + V_{\text{temp}} (1.01) + \overset{\text{offset}}{9\text{mV}} \times 101.005$$

$$@ V_2 - V_1 = 25\text{mV} \times 1.4463$$

(10)

$$V_o = 101.005 \times 25 \text{ mV} \times 1.4465 + \frac{5 \times 101}{2} + 9 \text{ mV} \times 101.005$$

$$= 7.086 \text{ V} \quad \left(\text{Assuming the amp doesn't saturate which it would} \right)$$

$$\text{error} = \frac{7.086 - 5}{5} \times 100\%$$

$$= 41.72\%$$



Entire system is 41.72 %


Just amp we use $V_1 - V_2 = 25 \text{ mV}$

$$\therefore V_o = 101.005 \times 25 \text{ mV} + \frac{5 \times 101}{2} + 9 \text{ mV} \times 101.005$$

$$= 5.95917 \text{ V}$$

$$\text{error} = 19.18\%$$

(11)

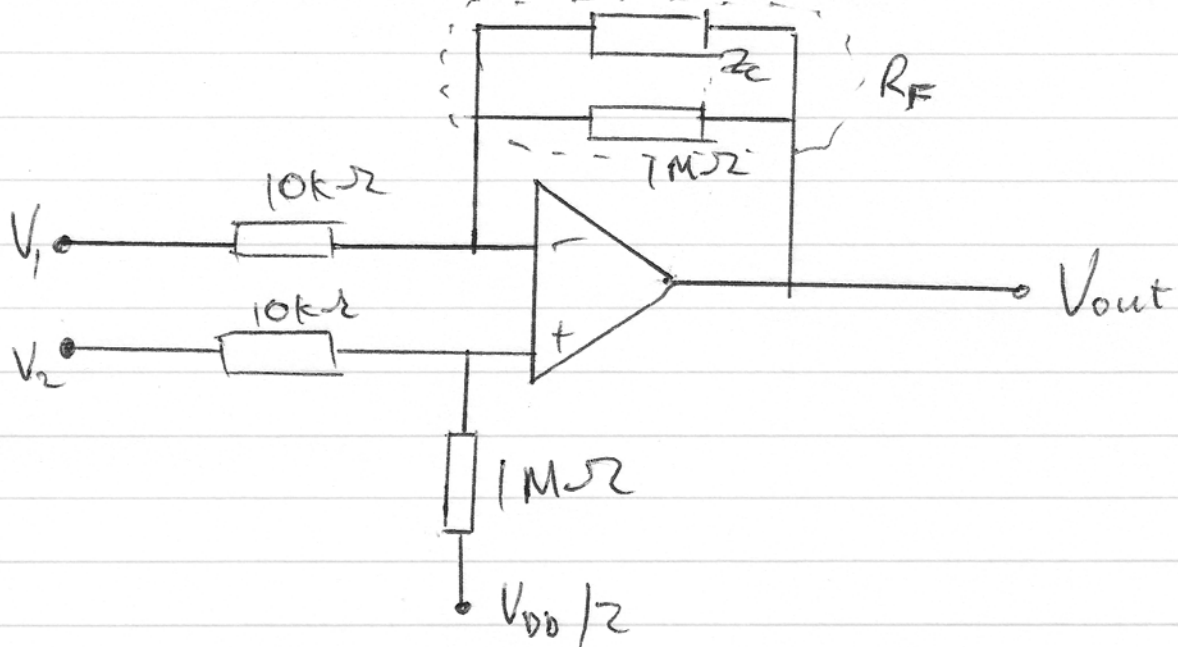Question 2I need -3dB @ 10kHz 

$$\frac{1}{R_F} = \frac{1}{Z_c} + \frac{1}{1\text{M}\Omega}$$

$$\frac{1}{R_F} = \frac{1\text{M}\Omega + Z_c}{1\text{M}\Omega Z_c}$$

$$R_F = \frac{1\text{M}\Omega \times Z_c}{1\text{M}\Omega + Z_c}$$

I need -3dB @ 10kHz

$$-3\text{dB} = 20(\log(x))$$


ie when $\text{Gain} = \frac{1}{\sqrt{2}}$

$$\frac{R_F}{10k\Omega} = \frac{1}{\sqrt{2}}$$

$$\frac{100\Omega \times \frac{1}{2\pi f C_{IN}}}{10k\Omega \left(100\Omega + \frac{1}{2\pi f C_{IN}} \right)} = \frac{1}{\sqrt{2}}$$

$$\therefore C_{IN} = 2.25 \times 10^{-9} \text{ F}$$

$$= 2.25 \text{ nF}$$

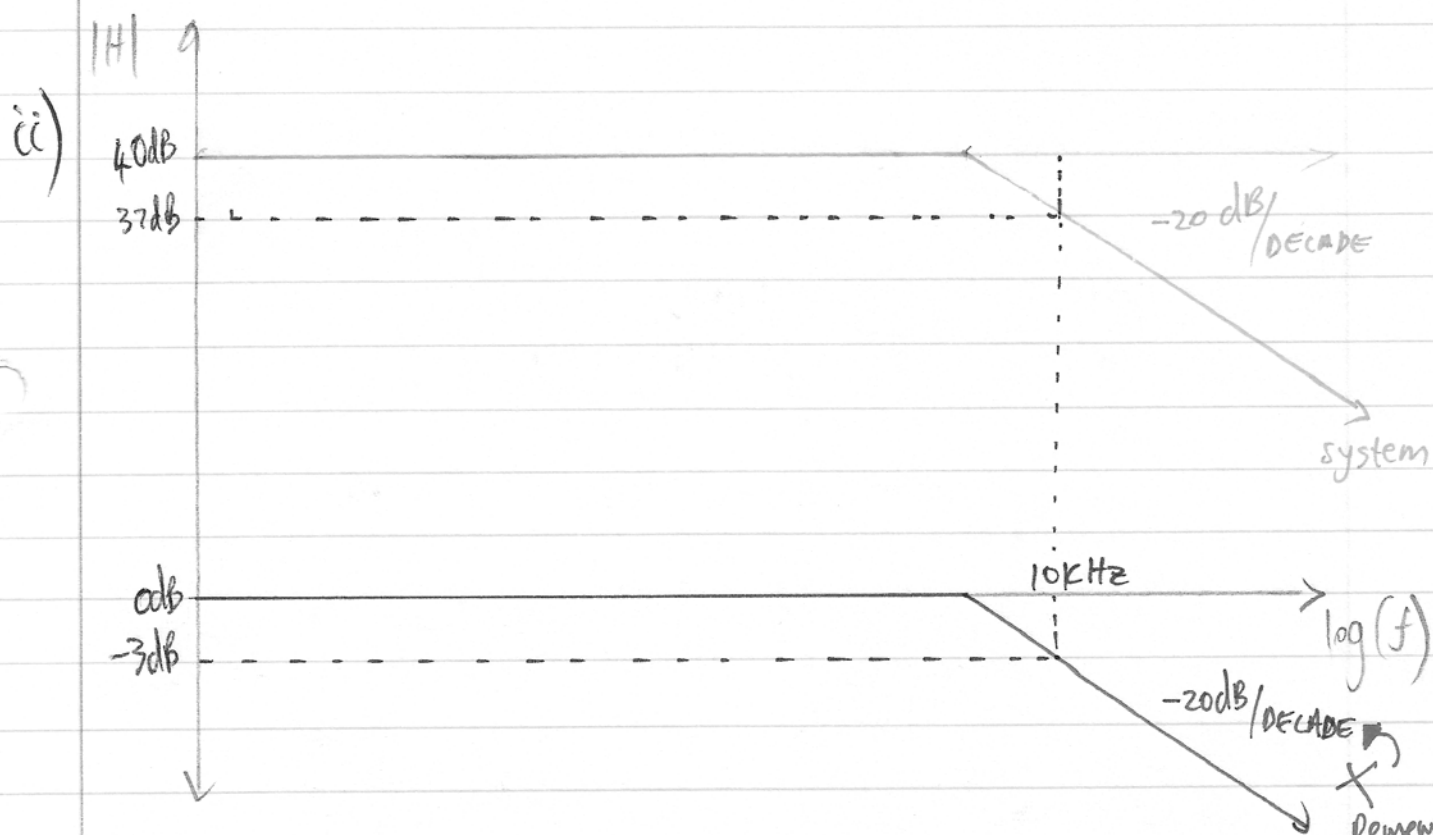

* ~~Remembering~~ 1st order Butterworth filter because that's what it is in figure 6.

Remember the amp is not the sensor the sensor has a bandwidth of 500MHz